

# Amateur Radio General License Training

Welcome to 2023 Amateur  
Radio General Class License  
Training


# Amateur Radio General License Training

**These presentations are sponsored by:**

**Mendocino Auxiliary Communications Service (MACS)**

**Mendocino County Amateur Radio Communications Service (McARCS)**

**Willits Amateur Radio Society (WARS)**

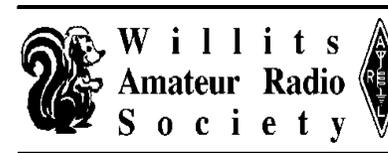

# Topics on General Class Exam

Section	Contents	Questions on Exam	Questions in Pool	Covered in Session
<b>G1</b>	FCC Rules and Regulations	5	57	<b>Session 5</b>
<b>G2</b>	Operating Procedures	5	50	<b>Session 4</b>
<b>G3</b>	Radio Wave Propagation	3	37	<b>Session 2</b>
<b>G4</b>	Amateur Radio Practices	5	60	<b>Session 3</b>
<b>G5</b>	Electrical Principles	3	40	<b>Session 1</b>
<b>G6</b>	Electronic Components	2	24	<b>Session 1</b>
<b>G7</b>	Practical Circuits	3	38	<b>Session 1</b>
<b>G8</b>	Signals and Emissions	3	43	<b>Session 3</b>
<b>G9</b>	Antennas and Feedlines	4	46	<b>Session 2</b>
<b>G0</b>	Safety	2	25	<b>Session 4</b>

# Sub-element G5 – electrical principles

## Topics in G5:

- **Electrical principles**
  - Reactance; inductance; capacitance; impedance; impedance transformation; resonance
  - The decibel; current and voltage dividers; electrical power calculations; sine wave root-mean-square (RMS) values; PEP calculations
  - Resistors, capacitors, and inductors in series and parallel; transformers
- **One question from each of the three categories on exam**

# Technician Electrical Review

- **Voltage (EMF) - force (pressure) that make electrons move**
  - Basic unit of EMF = volt, “E” in equations
- **Flow of electrons in an electrical circuit is current**
  - Basic unit of current = ampere, “I” in equations
- **Property opposing flow of electrons is electrical resistance**
  - Basic unit of resistance = ohm, “R” in equations

# Technician Electrical Review

## DC vs AC

- **Direct current (DC) flows in one direction**
- **Alternating current (AC) alternates between positive and negative directions**
  - Frequency (Hertz) = times per second that a cycle (+/-) is completed
  - Opposition to AC flow = impedance
  - Basic unit of impedance = ohm

# Technician Electrical Review

## Ohm's Law

- **Defines relationship between current, voltage, resistance**
  - With fixed resistance, current increases as voltage increases
  - With fixed voltage, current decreases as resistance increases
  - *Voltage "E" equals current "I" multiplied by resistance "R" ( $E = I \times R$ )*
  - *Current "I" equals voltage "E" divided by resistance "R" ( $I = E/R$ )*
  - *Resistance "R" equals voltage "E" divided by current "I" ( $R = E/I$ )*

# Technician Electrical Review

## Power

- **Rate at which electrical energy is used**

- Basic unit of electrical power = Watt (P)

Power “P” equals current “I” multiplied by voltage “E” (  $P = I \times E$  )

- $E = P / I$

- $I = P / E$

# Technician Electrical Review

## Power

### Changes in power levels expressed in decibels (dB)

- Doubling power = +3 dB change (*from 5W to 10W = +3 dB*)
- Halving power = -3 dB change
- -1 dB = 20.6% loss of power
- Pages 4-2 through 4-5 in ARRL study guide

# DC power calculations

## Three questions in pool

- Need to apply Ohm's law for two

$$(E = I \times R) = (I = E/R) = (R = E / I)$$

$$E = 12 \text{ V}, I = 0.2 \text{ A}, P = ? \text{ watts } P = I \times E = 12 \times 0.2 = \mathbf{2.4 \text{ W}}$$

$$E = 400 \text{ V}, R = 800 \ \Omega, P = ? \text{ watts } I = E/R, P = (E/R) \times E = E^2/R = 160000/800 = \mathbf{200 \text{ W}}$$

$$I = 7 \text{ mA}, R = 1250 \ \Omega, P = ? \text{ watts } E = I \times R, P = I \times (I \times R) = I^2 \times R = 0.007^2 \times 1250 = 0.061 \text{ W} = \mathbf{61 \text{ mW}}$$

# AC power calculations

## How to calculate power with changing voltage?

- Reference peak voltage
- Reference peak-to-peak voltage (2X peak)
- “Average” for sine wave = root mean square (RMS) value
  - $V_{RMS} = 0.707 \times V_{PK}$     $V_{RMS} = 0.707 \times 17 V_{PK} = \mathbf{12 V_{RMS}}$
  - $V_{RMS} = 0.707 \times (V_{P-P} / 2)$
  - $V_{P-P} = 2 \times 1.414 \times V_{RMS}$     $V_{P-P} = 2 \times 1.414 \times 120 V_{RMS} = \mathbf{339.4 V_{P-P}}$
- Power dissipated by resistor at  $V_{RMS}$  = power at equal DC voltage

# AC power calculations

## How to calculate peak envelope power (PEP)

- PEP = average power of one full RF cycle at envelope peak
- $PEP \text{ (watts)} = V_{RMS}^2 / \text{impedance}$
- **PEP = average power** in absence of amplitude modulation (ratio = 1.0)
- To calculate PEP given  $V_{P-P}$  first convert to  $V_{RMS}$ 
  - **(G5B14)**  $V_{RMS} = 0.707 \times (V_{P-P} / 2) = 0.707 \times (500V_{P-P} / 2) = 176.75 V_{RMS}$
  - $PEP = V_{RMS}^2 / \Omega = (176.75)^2 / 50 = \mathbf{675 W_{PEP}}$
  - **(G5B06)**  $V_{RMS} = 0.707 \times (V_{P-P} / 2) = 0.707 \times (200 V_{P-P} / 2) = 70.7 V_{RMS}$
  - $PEP = V_{RMS}^2 / \Omega = (70.7)^2 / 50 = \mathbf{100 W_{PEP}}$
- To calculate  $V_{RMS}$  given PEP and impedance  $V_{RMS} = \sqrt{PEP \times R}$ 
  - **(G5B12)**  $V_{RMS} = \sqrt{1200 \times 50} = \sqrt{60000} = \mathbf{245 V_{RMS}}$

# Section questions:

*G5B03*

**How many watts of electrical power are consumed if 400 VDC is supplied to an 800-ohm load?**

- A. 0.5 watts
- B. 200 watts
- C. 400 watts
- D. 3200 watts

# Section questions:

*G5B01*

**What dB change represents a factor of two increase or decrease in power?**

- A. Approximately 2 dB
- B. Approximately 3 dB
- C. Approximately 6 dB
- D. Approximately 9 dB

# Section questions:

*G5B08*

**What is the peak-to-peak voltage of a sine wave with an RMS voltage of 120 volts?**

- A. 84.8 volts
- B. 169.7 volts
- C. 240.0 volts
- D. 339.4 volts

# Section questions:

*G5B11*

**What is the ratio of PEP to average power for an unmodulated carrier?**

- A. 0.707
- B. 1.00
- C. 1.414
- D. 2.00

# Impedance and Reactance

## Impedance

- Opposition to AC current flow in a circuit is impedance
- Defined the ratio of voltage to current, measured in ohms
- Inverse of impedance is admittance

## Reactance

- Inductors and capacitors respond differently to AC vs DC
- Both oppose flow of AC
- Property known as reactance, measured in ohms, “X” in formulas
- Inductive reactance  $X_L$  increases as frequency increases
- Capacitive reactance  $X_C$  decreases as frequency increases

# Resonance

## LC circuits

- Inductors and capacitors can be combined in “LC” circuits
- May be in parallel or series
- Resonance occurs at frequency where  $X_L = X_C$  and they cancel
- Impedance is very low at resonance in series LC circuit

## Transformers

- Two inductors with over-lapping magnetic field (mutual inductance)
- Used to “transform” AC voltage or impedance, up or down
- Change in voltage/impedance proportional to ratio of primary to secondary windings
- Voltage appearing across secondary winding = primary voltage x turns ratio
- 1:4 step-up transformer 10 VAC on primary yields 40 VAC across secondary
- Power equal on both sides, higher current in primary of step-up vs secondary
- Function even if connected “backwards”
- 500 turn primary/1500 turn secondary = 1:3 120 VAC primary = 360 VAC secondary

# Transformers

## Impedance transformation

- Turns ratio  $N_p / N_s = \sqrt{Z_p / Z_s}$
- Match 600  $\Omega$  feed point to 50  $\Omega$  coax  $N_p / N_s = \sqrt{600/50} = \sqrt{12} = 3.5:1$
- RF impedance match with transformer, Pi-network, length of transmission line

# Section questions:

*G5A08*

**What is impedance?**

- A. The ratio of current to voltage
- B. The product of current and voltage
- C. The ratio of voltage to current
- D. The product of current and reactance

# Section questions:

*G5A12*

**What occurs in an LC circuit at resonance?**

- A. Current and voltage are equal
- B. Resistance is cancelled
- C. The circuit radiates all its energy in the form of radio waves
- D. Inductive reactance and capacitive reactance cancel

# Section questions:

*G5A06*

## **How does a capacitor react to AC?**

- A. As the frequency of the applied AC increases, the reactance decreases
- B. As the frequency of the applied AC increases, the reactance increases
- C. As the amplitude of the applied AC increases, the reactance increases
- D. As the amplitude of the applied AC increases, the reactance decreases

# Section questions:

*G5C06*

**What is the voltage output of a transformer with a 500-turn primary and a 1500-turn secondary when 120 VAC is applied to the primary?**

- A. 360 volts
- B. 120 volts
- C. 40 volts
- D. 25.5 volts

# Section questions:

*G5A11*

**What letter is used to represent reactance?**

- A. Z
- B. X
- C. B
- D. Y

# Unit Conversion

## Unit multipliers and conversion

- The actual value of a component or unit of measure may be several times greater, or only a small fraction of the base unit
- Frequencies may be in the millions of Hertz
- Capacitance may be in millionths of a Farad
- Unit multipliers used to simplify measurement

<i>pico</i>	=	<i>1 trillionth</i>	<i>multiplier 10<sup>-12</sup></i>
<i>micro</i>	=	<i>1 millionth</i>	<i>multiplier 10<sup>-6</sup></i>
<i>milli</i>	=	<i>1 thousandth</i>	<i>multiplier 10<sup>-3</sup></i>
<i>kilo</i>	=	<i>thousand</i>	<i>multiplier 10<sup>3</sup></i>
<i>mega</i>	=	<i>million</i>	<i>multiplier 10<sup>6</sup></i>
<i>giga</i>	=	<i>billion</i>	<i>multiplier 10<sup>9</sup></i>

# Like Components in Series/Parallel

## **Series circuits**

- Components connected end to end
- Same DC current flows through all components

## **Parallel circuits**

- Components connected side by side
- Same voltage appears across all components

# Like Components in Series/Parallel

## Resistors in parallel

- Total current is equal to the sum of the current through each resistor
- 10Ω, 20Ω, and 50Ω resistors in parallel, with 10V applied
- Current = 1.0A + 0.5A + 0.2A = 1.7A, effective R = E/I = 10/1.7 = **5.9Ω**
- Note effective resistance lower than any individual resistor
- Two resistors in parallel  $R_{EQU} = (R_1 \times R_2)/(R_1 + R_2)$
- *100Ω + 200Ω resistors in parallel*  $R_{EQU} = (100 \times 200)/(100+200) = 20000/300 = \mathbf{66.6\Omega}$
- Three resistors in parallel  $R_{EQU} = 1/(1/R_1 + 1/R_2 + 1/R_3)$
- 10Ω, 20Ω, and 50Ω resistors in parallel
- $R_{EQU} = 1/(1/10 + 1/20 + 1/50) = 1/(0.1 + 0.05 + 0.02) = 1/0.17 = \mathbf{5.9\Omega}$

# Like Components in Series/Parallel

## Resistors in series

- Much simpler, series resistance is additive
- $10\Omega$ ,  $20\Omega$ , and  $50\Omega$  resistors in series,  $R_{EQU} = R_1 + R_2 + R_3 = 10 + 20 + 50 = \mathbf{80\Omega}$

## Inductors

- Same as resistors, two inductors in series  $L_{EQU} = L_1 + L_2$
- $20\text{ mH}$  in series with a  $50\text{ mH} = 20 + 50 = \mathbf{70\text{ mH}}$
- Three inductors in parallel  $L_{EQU} = 1/(1/L_1 + 1/L_2 + 1/L_3)$
- Three  $10\text{ mH}$  inductors in parallel
- $L_{EQU} = 1/(1/10 + 1/10 + 1/10) = 1/(0.3) = \mathbf{3.3\text{ mH}}$

# Like Components in Series/Parallel

## Capacitors

Opposite from resistors and inductors

Additive when connected in parallel

- Three capacitors in parallel  $C_{EQU} = C_1 + C_2 + C_3 = 5 + 5 + 0.75 = \mathbf{10.750\ nF}$

Reduced when connected in series

- Two capacitors in series  $C_{EQU} = (C_1 \times C_2)/(C_1 + C_2)$
- $C_{EQU} = (20 \times 50)/(20+50) = 1000/70 = \mathbf{14.8\ \mu F}$
- Three capacitors in series  $C_{EQU} = 1/(1/C_1 + 1/C_2 + 1/C_3)$
- $C_{EQU} = 1/(1/100 + 1/100 + 1/100) = 1/(0.003) = \mathbf{33.3\ \mu F}$

# Like Components in Series/Parallel

## Shortcuts to remember:

Resistors/inductors in parallel or capacitors in series

- If all components are equal value, divide value of one component by the total number of components
- Four  $100\Omega$  in parallel  $R_{\text{EQU}} = 100/4 = 25\Omega$
- Three  $100\ \mu\text{F}$  capacitors in series  $C_{\text{EQU}} = 100/3 = 33.3\ \mu\text{F}$

To add inductance to a circuit, add inductor in series

To add capacitance to a circuit, add a capacitor in parallel

# Section questions:

*G5C10*

**What is the inductance of three 10-millihenry inductors connected in parallel?**

- A. 0.30 henries
- B. 3.3 henries
- C. 3.3 millihenries
- D. 30 millihenries

# Section questions:

*G5C03*

**What is the total resistance of a 10-, a 20-, and a 50-ohm resistor connected in parallel?**

- A. 5.9 ohms
- B. 0.17 ohms
- C. 17 ohms
- D. 80 ohms

# Section questions:

*G5C05*

**Why is the primary winding wire of a voltage step-up transformer usually a larger size than that of the secondary winding?**

- A. To improve the coupling between the primary and secondary
- B. To accommodate the higher current of the primary
- C. To prevent parasitic oscillations due to resistive losses in the primary
- D. To ensure that the volume of the primary winding is equal to the volume of the secondary winding

# Section questions:

*G5C01*

**What causes a voltage to appear across the secondary winding of a transformer when an AC voltage source is connected across its primary winding?**

- A. Capacitive coupling
- B. Displacement current coupling
- C. Mutual inductance
- D. Mutual capacitance

# Amateur Radio General License Training

End of G5 Electrical Principles